



MANIPAL ACADEMY OF HIGHER EDUCATION

BTech II Semester MIDSEM Examination March 2025
FUNDAMENTALS OF ELECTRONICS [ECE 1072-PHY]

SCHEME OF VALUATION

⑥ Assuming 'M1' in saturation:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$
$$= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{2}{0.18} (1 - 0.5)^2 = 277.77 \mu A$$
$$V_{DS} = V_{DD} - I_D R_D = 1.8 - 277.77 \times 10^{-6} \times 2 \times 10^3 = 1.24 V$$
$$V_{GS} - V_{TH} = 1 - 0.5 = 0.5 V$$

Since $V_{DS} > V_{GS} - V_{TH}$, 'M1' is in saturation → 1 MARK

Drain current derivation → 2 MARKS
 $V_{DS} - I_D$ characteristics → 1 MARK

7 $I_0 = 1 \text{ pA}$ at 20°C
 $I_D = ?$ 150°C , $V_D = 0.5 \text{ V}$
 $r_d = ?$ 150°C

$$I_0' = I_0 \cdot 2^{\frac{150-20}{10}}$$

$$I_0' = 1 \text{ p} \cdot 2^{13}$$

$$\boxed{I_0' = 8.192 \text{ nA}} \quad \text{--- } \frac{1}{2} \text{ M}$$

$$V_T = \frac{T}{11600} = \frac{150 + 273}{11600} = \frac{423}{11600} = 36.465 \text{ mV}$$

$$\text{--- } \frac{1}{2} \text{ M}$$

$$I_D = I_0' \left[e^{\frac{V_D}{\eta V_T}} - 1 \right]$$

⊗ Assume diode is Ge, $\eta = 1$

$$I_D = 8.192 \text{ n} \left[e^{\frac{0.5 \times 11600}{423}} - 1 \right]$$

$$\boxed{I_D = 7.383 \text{ mA}} \quad \text{--- } 1 \text{ M}$$

$$r_d = \frac{\eta V_T}{I_0' + I_D} = \frac{1 \times 36.465 \text{ m}}{8.192 \text{ n} + 7.383 \text{ mA}} = 4.939 \Omega \text{ --- } 1 \text{ M}$$

⊗ Assume diode is Si, $\eta = 2$

$$I_D = 8.192 \text{ n} \left[e^{\frac{0.5 \times 11600}{2 \times 423}} - 1 \right]$$

$$\boxed{I_D = 7.768 \mu\text{A}} \quad \text{--- } 1 \text{ M}$$

$$r_d = \frac{2 \times 423}{(8.192 \text{ n} + 7.768 \mu) \times 11600} = 9.378 \text{ k}\Omega \text{ --- } 1 \text{ M}$$

NOTE: Based on the decimal points taken, diode current and resistance can vary. Please consider the diode current and resistance values with $\pm(10 \text{ to } 15)\%$ tolerance while evaluating the answer scripts.

$$\textcircled{8} \quad I_{L_{\max}} = -I_{Z_{\min}} + I_T = -0.2 \times 10^{-3} + \frac{10 - 10}{10}$$

$$I_{L_{\max}} = 200 \times 10^{-3} - 0.2 \times 10^{-3} = 199.8 \times 10^{-3}$$

$$R_{L_{\min}} = \frac{V_Z}{I_{L_{\max}}} = \frac{10}{199.8 \times 10^{-3}} = 50.05 \Omega = P/V_Z$$

1.5 MARKS

$$I_{L_{\min}} = I_T - I_{Z_{\max}} = 200 \times 10^{-3} - 1 \times 10^{-1} = 100 \times 10^{-3}$$

$$R_{L_{\max}} = \frac{10}{100 \times 10^{-3}} = 100 \Omega$$

1.5 MARKS

9. primary

$$V_{\text{rms}} = 210 \text{ V} \Rightarrow V_{\text{peak}} = 210\sqrt{2}$$

$$V_{\text{peak}} = 296.98 \text{ V}$$

Secondary

$$V_m = V_{\text{peak}}/10$$

$$V_m = 29.698 \text{ V}$$

(a) $V_{\text{dc}} = \frac{V_m}{\pi} = \frac{29.698}{\pi} = 9.453 \text{ V}$ - 1/2 M

(b) $\eta = \frac{P_{\text{dc}}}{P_{\text{ac}}} = \frac{(V_{\text{dc}})^2}{(V_{\text{rms}})^2} = 0.405\%$

$$V_{\text{rms}} = \frac{V_m}{2} = 14.849 \text{ V}$$
 - 1/2 M

(c) PIV = $V_m = 29.698 \text{ V}$ - 1/2 M

(d) $V_{\text{dc}} = \left(\frac{2fCR_L}{1 + 2fCR_L} \right) V_m$
(with C-filter)


$$= \left(\frac{2 \times 60 \times 1 \text{ m} \times 1 \text{ k}}{1 + 2 \times 60 \times 1 \text{ m} \times 1 \text{ k}} \right) 29.69$$

$$V_{\text{dc}} = 29.452 \text{ V}$$
 - 1/2 M

(e) $I_{\text{rms}} = \frac{V_{\text{rms}}}{R_L} = 14.849 \text{ mA}$ - 1/2 M

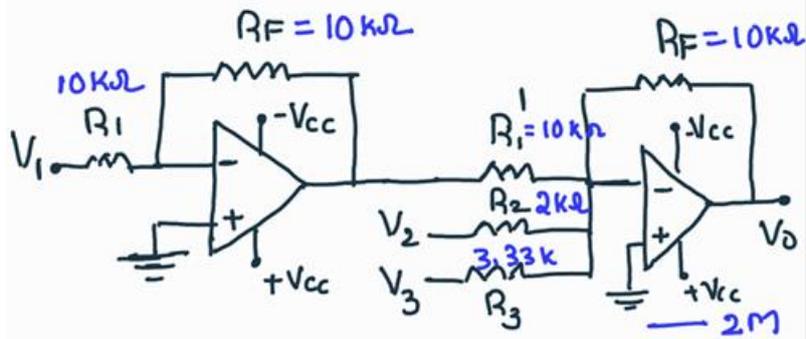(f) $f_o = f_i = 60 \text{ Hz}$ - 1/2 M

10 $V_0 = V_1 - 5V_2 - 3V_3$, $R_F = 10k\Omega$



$$\frac{R_F}{R_1} = 1$$

$$R_1 = 10k\Omega \quad -\frac{1}{2}M$$

$$\frac{R_F}{R_1'} = 1 \Rightarrow R_1' = 10k\Omega \quad -\frac{1}{2}M$$

$$\frac{R_F}{R_2} = 5 \Rightarrow R_2 = 2k\Omega \quad -\frac{1}{2}M$$

$$\frac{R_F}{R_3} = 3 \Rightarrow R_3 = 3.33k\Omega \quad -\frac{1}{2}M$$

(ii) $V_{DD} - I_D R_D = V_G - V_{TH} = \frac{V_{DD} R_2}{R_1 + R_2} - V_{TH}$

$$1.8 - I_D (3 \times 10^3) = \frac{1.8 \times 12 \times 10^3}{17 \times 10^3} - 0.4$$

$$I_D = \frac{1.8 - 0.87}{3 \times 10^3} = 0.31 \text{ mA}$$

1 MARK

$$V_{GS} = V_G - V_S = \frac{1.8 \times 12 \times 10^3}{17 \times 10^3} - 0.31 \times 10^{-3} \times 1 \times 10^3$$

$$V_{GS} = 0.96 \text{ V}$$

1 MARK

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_{\max} (V_{GS} - V_{TH})^2$$

$$0.31 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right) (0.96 - 0.4)^2$$

$$\left(\frac{W}{L}\right)_{\max} = 19.77$$

1 MARK


(12)

$$A_d = \frac{V_o}{V_1 - V_2} = \frac{10}{2 \times 10^{-3}} = 5000 \rightarrow 0.5 \text{ MARKS}$$

$$A_c = \frac{V_o}{\frac{V_1 + V_2}{2}} = \frac{5 \times 10^{-3}}{0.5 \times 10^{-3}} = 10 \rightarrow 0.5 \text{ MARKS}$$

$$CMRR = \left| \frac{A_d}{A_c} \right| = \frac{5000}{10} = 500 \rightarrow 1 \text{ MARK}$$

(13)

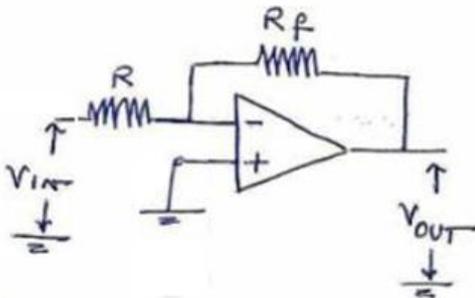

NON-INVERTING AMPLIFIER CIRCUIT \rightarrow 1 MARK

$$A_v = \frac{R_F}{R}$$

$$10 = \frac{R_F}{R} \Rightarrow R = \frac{R_F}{10} = 1 \text{ k}\Omega \rightarrow 1 \text{ MARK}$$

(14)

During both the half cycles of V_{in} diode conducts.

$$\therefore V_o = 5 \sin \omega t + 5 \rightarrow 1 \text{ MARK}$$

$$V_{DC} = 5 \text{ V}$$

$$I_{DC} = \frac{5}{1 \times 10^3} = 5 \text{ mA} \rightarrow 1 \text{ MARK}$$