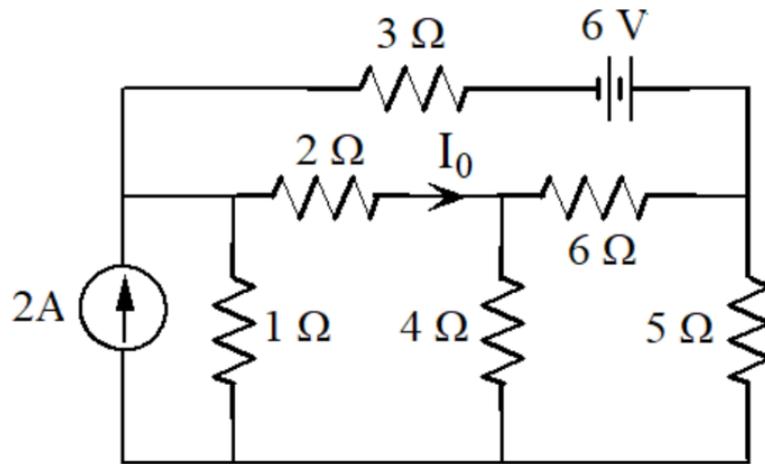


Type: DES

11A. Using superposition principle, determine the current I_0 as shown. 4M



With 6 V source alone

$$\begin{bmatrix} 7 & -4 & -2 \\ -4 & 15 & -6 \\ -2 & -6 & 11 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 6 \end{bmatrix}$$

$$i_1 = 0.5674 \text{ A}, \quad i_2 = 0.5254 \text{ A}, \quad i_3 = 0.9352 \text{ A}$$

$$I_{0:6V} = (i_1 - i_3) = -0.3678 \text{ A} \quad \text{--- 1.5 M}$$

With 2 A source alone


$$\begin{bmatrix} 7 & -4 & -2 \\ -4 & 15 & -6 \\ -2 & -6 & 11 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix}$$

$$i_1 = 0.45184 \text{ A}, \quad i_2 = 0.19615 \text{ A}, \quad i_3 = 0.18914 \text{ A}$$

$$I_{0:2A} = (i_1 - i_3) = 0.2627 \text{ A} \quad \text{--- 1.5 M}$$

$$I_0 = I_{0:6V} + I_{0:2A} = -0.1051 \text{ A} \quad \text{--- 1 M}$$

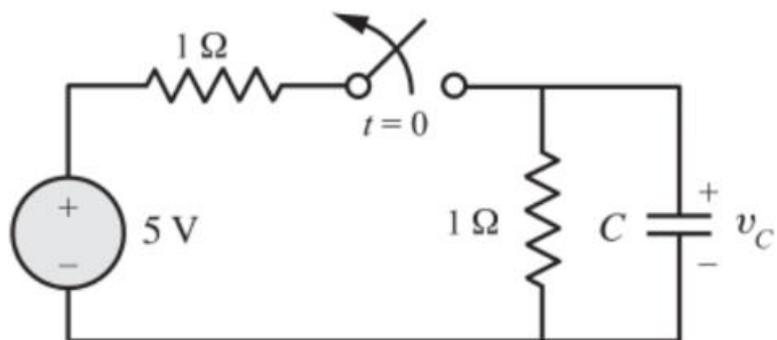11B. For the circuit shown, assume that the switch was in closed state for a long time. At $t = 0$, it is operated as shown. Obtain $V_c(t)$ for $t > 0$. Also calculate the time when capacitor voltage becomes 1.25 V. 3M



$$v_c(0^-) = v_c(0) = v_c(0^+) = 2.5 \text{ V} \quad \text{--- 0.5 M}$$


$$v_c(\infty) = 0 \text{ V} \quad \text{--- 0.5 M}$$

$$\tau = RC = C \text{ s} \quad \text{--- 0.5 M}$$

$$v_c(t) = 2.5 e^{-t/c} \text{ V} \quad \text{--- 0.5 M}$$

$$t = 0.693 C \text{ s for } v_c(t) = 1.25 \text{ V} \quad \text{--- 1 M}$$

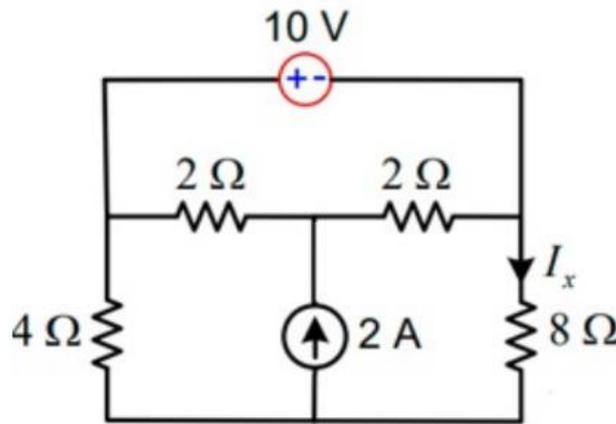11 C. Determine the current I_x in the given network using nodal analysis 3M



$$V_A - V_C = 10 \dots\dots\dots (0.5)$$

$$(V_A - V_B)/2 + V_A/4 + (V_C - V_B)/2 + V_C/8 = 0 \quad \dots\dots\dots (0.5)$$


$$(V_B - V_A)/2 + (V_B - V_C)/2 = 2 \quad \dots\dots\dots(0.5)$$

On solving above three equations: $\dots\dots\dots(0.5)$


$$V_C = -4/3 \text{ V} \quad \dots\dots\dots(0.5)$$

$$I = -0.166 \text{ A} \quad \dots\dots\dots(0.5)$$

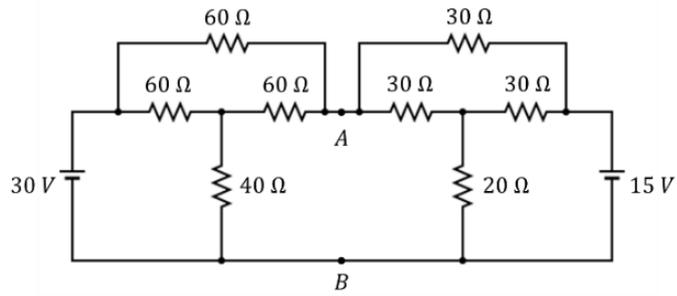
12 A. Find Thevenin's equivalent of the network across terminals A and B. If any value whatsoever may be selected for load resistance across terminals A and B, what is the maximum power that could be dissipated in it? 4M



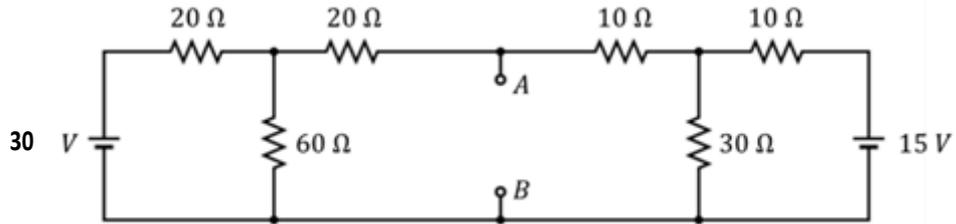
Converting 60 ohm – 60 ohm – 60 ohm delta to star and 30 ohm – 30 ohm – 30 ohm delta to star,



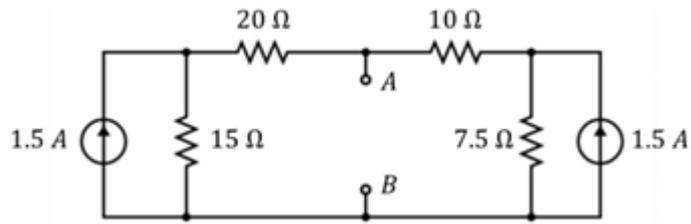Converting practical voltage sources to practical current sources and simplifying,



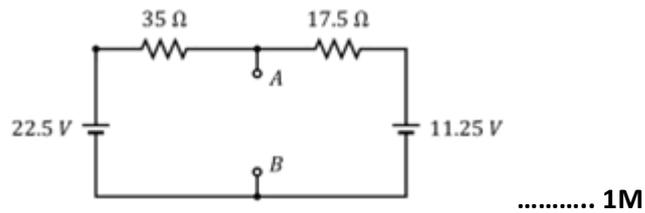Converting practical current sources to practical voltage sources and simplifying,



..... 1M

Current in the circuit will be,

$$I = \frac{22.5 - 11.25}{35 + 17.5} = 0.2142 \text{ A}$$

..... 1M

Thevenin's voltage and resistance will be,

$$V_{th} = V_{AB} = 11.25 + (17.5 \times 0.2142) = 15 \text{ V}$$

$$R_{th} = 11.67 \Omega$$

..... 1M

Maximum power dissipated is,

$$P_{max} = \frac{V_{th}^2}{4R_{th}} = 4.82 \text{ W}$$

..... 1M

12 B. A series circuit of resistance of 10Ω , an inductance of 13 mH are connected in series. A supply of 100 V at 50 Hz is given to the circuit. Find the impedance, current, power factor and power consumed in the circuit. 3M

A series circuit of resistance of **10Ω** , an inductance of **13 mH** and a capacitance of **$150 \mu\text{F}$** connected in series. A supply of **100 V** at **50 Hz** is given to the circuit. Find the impedance, current, power factor and power consumed in the circuit.

$$X_L = 2\pi fL = 4.0841 \Omega$$

$$X_C = \frac{1}{2\pi fC} = 21.2207 \Omega$$

$$Z = R + j(X_L - X_C) = 10 - j 17.1366 \Omega = 19.8409 \angle -59.7345^\circ \Omega \quad \text{--- 1 M}$$

$$|I| = \frac{V_s}{|Z|} = 5.0401 \text{ A}$$


$$\Phi = \tan^{-1}\left(\frac{X_C - X_L}{R}\right) = 59.7345^\circ$$

$$I = |I| \angle \Phi = 5.0401 \angle 59.7345^\circ \text{ A} = 2.5402 + j 4.3531 \text{ A} \quad \text{--- 1 M}$$

$$\text{Power factor} = \cos \Phi = 0.5040 \text{ (Leading)} \quad \text{--- 0.5 M}$$

$$\text{Power consumed} = |V_s||I|\cos\Phi = 254.0210 \text{ W} \quad \text{--- 0.5 M}$$

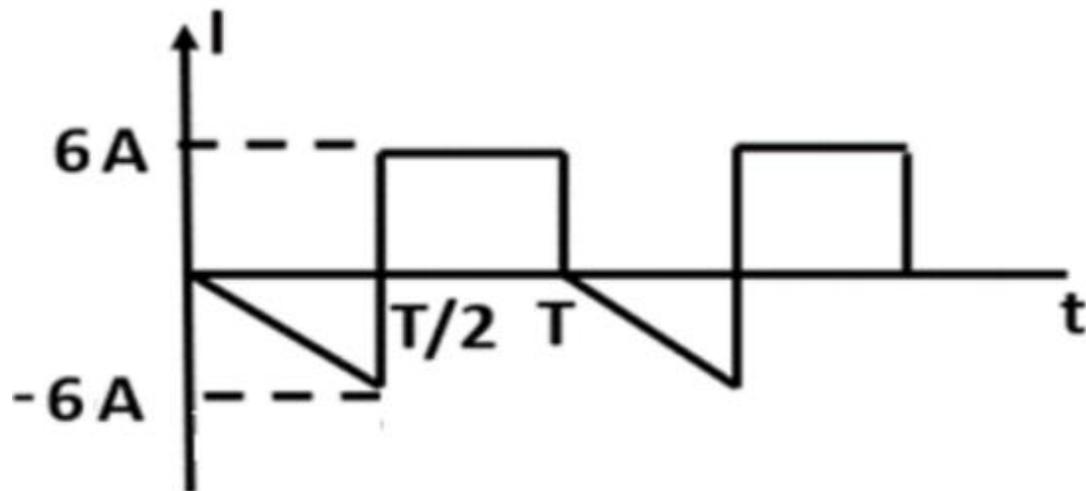12 C. Find the average and RMS value of the voltage waveform shown below. 3M



$$i(t) = -\frac{12t}{T} \quad 0 < t < T/2 \quad \text{--- 0.5 M}$$

$$i(t) = 6 \quad T/2 < t < T \quad \text{--- 0.5 M}$$

$$i_{\text{avg}} = \frac{1}{T} \left[\int_0^{T/2} -\frac{12t}{T} dt + \int_{T/2}^T 6 dt \right] = 1.5 \text{ A} \quad \text{--- 1 M}$$

$$i_{\text{RMS}} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} \left(-\frac{12t}{T} \right)^2 dt + \int_{T/2}^T 6^2 dt \right]} = 4.899 \text{ A} \quad \text{--- 1 M}$$