



Mid Semester Test – Answer Scheme

Course: Fundamentals of Electrical Engineering

Date & Time: 7 March 2025, 04:30 – 06:00 PM

Course Code: ELE 1072

Part A – Objective Questions

1. C. 63.2, final
2. B. $(6.5 - j18.9) \Omega$
3. A. 100 V
4. B. K
5. C. 90°


Part B – Descriptive Questions

6. The circuit is redrawn as shown:

$$\begin{bmatrix} 12 & -6 & 0 \\ -6 & 18 & 6 \\ 0 & 6 & 18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 6 \\ 0 \\ 18 \end{bmatrix} \text{----- } 3 \times 1 = 3 \text{ marks}$$

Solving we get, $I_1 = 0.3846 \text{ A}$ ----- 1 mark

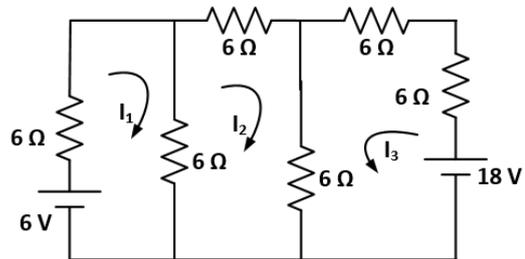$\therefore P_{6V} = 6 \times I_1 = 2.3076 \text{ W}$ ----- 1 mark




7. To find V_{Th} ,

Applying node voltage method,


$$\begin{bmatrix} \left(\frac{1}{6} + \frac{1}{6} + \frac{1}{2}\right) & -\frac{1}{6} & -\frac{1}{6} \\ -\frac{1}{6} & \left(\frac{1}{6} + \frac{1}{6}\right) & -\frac{1}{6} \\ -\frac{1}{6} & -\frac{1}{6} & \left(\frac{1}{2} + \frac{1}{6} + \frac{1}{6}\right) \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} 6 \\ 6 \\ 0 \end{bmatrix}$$

----- $3 \times 0.5 = 1.5$ marks

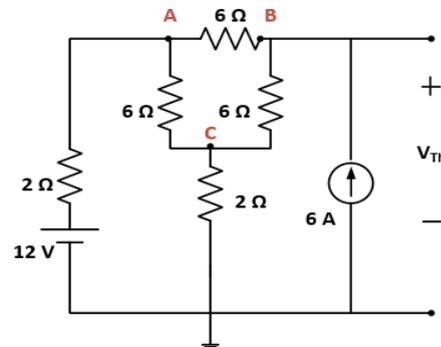Solving we get, $V_B = V_{Th} = 30 \text{ V}$ ----- 0.5 mark



To find R_{Th}

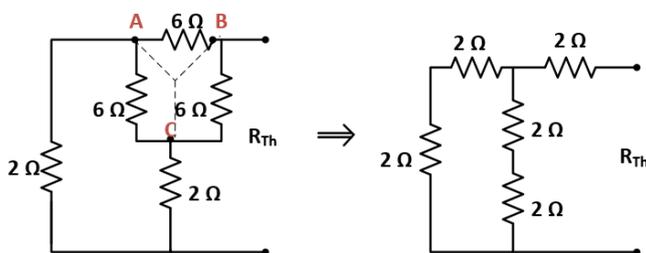

$\Rightarrow R_{Th} = 4 \Omega$ ----- 2 marks

$\therefore P_{max} = \frac{V_{Th}^2}{4R_{Th}} = 56.25 \text{ W}$ ----- 1 mark



8. Voltage leading the current by $45^\circ \Rightarrow \angle Z = 45^\circ$ ----- 1 mark

Total impedance = $Z = R + (jX_L || -jX_C) = R + j \frac{X_L X_C}{X_L - X_C}$ ----- 1 mark

$\therefore 45 = \tan^{-1} \left(\frac{X_L X_C}{R(X_L - X_C)} \right) \Rightarrow X_C = 8.5714 \Omega$ ----- 2 marks

$\therefore C = 116.66 \mu F$ ----- 1 mark

9. From the power triangle,

$\tan(\phi_{old}) = \frac{Q_{old}}{P} \Rightarrow Q_{old} = 3750 \text{ var}$ ----- 2 marks

Similarly,

$\tan(\phi_{new}) = \frac{Q_{new}}{P} \Rightarrow Q_{new} = 2421.61 \text{ var}$


----- 1 mark

$\therefore Q_C = Q_{old} - Q_{new} \Rightarrow Q_C = 1328.38 \text{ var}$

----- 1 mark

$Q_C = \frac{V^2}{X_C} \Rightarrow X_C = 36.43 \Omega \Rightarrow C = 87.36 \mu F$

----- 1 mark

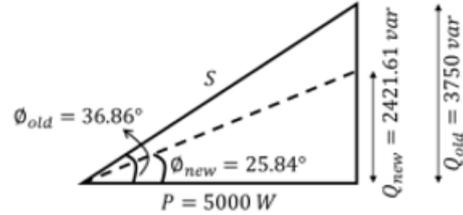

10. Given, $\bar{V}_L = 400 \angle 0^\circ \text{ V} \Rightarrow \bar{V}_{ph} = 230.94 \angle -30^\circ \text{ V}$

$\therefore \hat{Z} = \frac{230.94 \angle -30^\circ}{10 \angle -66.86^\circ} \Rightarrow \hat{Z} = 23.09 \angle 36.86^\circ \Omega$ ----- 1 mark

$\therefore R = |Z| \cos \theta = 18.474 \Omega$ ----- 0.5 mark

$X_L = |Z| \sin \theta = 13.85 \Omega \Rightarrow L = 44.08 \text{ mH}$ ----- 0.5 mark

Power factor = $\cos \theta = 0.8$ lagging ----- 0.5 mark

$P = 3V_{ph}I_{ph} \cos \theta = 5542.56 \text{ W}$ ----- 1 mark

$Q = 3V_{ph}I_{ph} \sin \theta = 4155.96 \text{ var}$ ----- 1 mark

$S = 3V_{ph}I_{ph} = 6928.2 \text{ VA}$ ----- 0.5 mark