

**Mid Semester Test (MISAC)**




Course:	Fundamentals of Electrical Engineering	Exam :	Mid Term, Marks: 30, Duration: 90 Min
Course Code:	ELE 1072	Date & Time:	7 March 2025, 04:30 – 06:00 PM
Semester:	Second (Sections – PA to PH)	Branch:	Physics Cycle

Part A – Objective Questions

Q. No.	Question	Marks	BTL	CO
1	During capacitor charging, the voltage rises to _____ percent of its _____ value after one time constant. A. 63.2, initial B. 37, initial C. 63.2, final D. 37, final	1	2	1
2	In an ac circuit, the supply voltage and resulting current are expressed by $v(t) = 100 \sin(100\pi t + 24^\circ)$ V and $i(t) = 5 \cos(100\pi t + 5^\circ)$ A. The impedance of the load is A. $(6.5 + j18.9) \Omega$ B. $(6.5 - j18.9) \Omega$ C. $(18.9 + j6.5) \Omega$ D. $(18.9 - j6.5) \Omega$	1	3	2
3	A series RLC circuit has a sinusoidal input voltage of 1 V. If $L = 100$ mH, $R = 10 \Omega$, and $C = 0.1 \mu\text{F}$, the magnitude of voltage across capacitor at resonance is 1. 100 V 2. 30 V 3. 15.91 V 4. 1 V	1	3	2
4	If all the elements of a delta connected resistive network are scaled by a factor k , where $k > 0$, then the elements of equivalent star connection will be scaled by a factor of ____ 1. k^2 2. k 3. $1/k$ 4. \sqrt{k}	1	3	1
5	A three-phase star connected balanced RYB supply has $V_{RY} = 400 \angle 30^\circ$ V. The angular difference between V_{BN} and V_{RY} is 1. 30° 2. 60° 3. 90° 4. 120°	1	4	2



Part B – Descriptive Questions

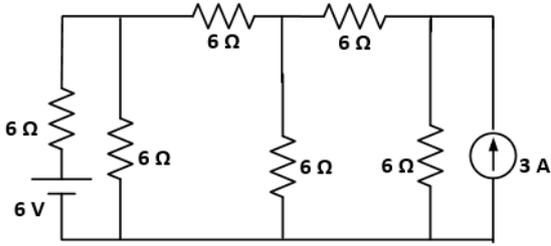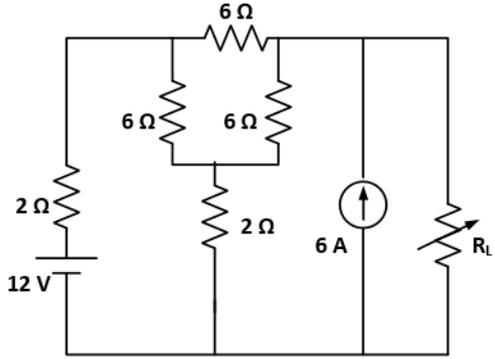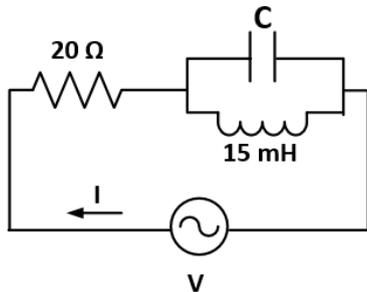Q. No.	Question	Marks	BTL	CO
6	<p>For the circuit shown, use mesh current analysis to determine the power delivered by the 6 V source.</p> 	5	3	1
7	<p>For the circuit shown below, calculate the maximum power transferred to the load resistor RL.</p> 	5	3	1
8	<p>A 20 Ω resistor is connected in series with a parallel combination of capacitance “C” and a pure inductance of 15 mH as shown in figure below. This circuit is connected to a voltage source of angular frequency $\omega = 1000 \text{ rad/s}$. Find the value of capacitance “C” such that the supply voltage is leading the current (I) by 45°.</p> 	5	4	2
9	<p>A 5 kW load at 0.8 lagging power factor is being supplied by a 220 V, 50 Hz, single-phase ac supply. Calculate the reactive power drawn from the source. If a capacitor is now connected in parallel to the load to improve the power factor to 0.9 lagging, find the value of the capacitor required.</p>	5	3	2
10	<p>Three similar coils when connected in star across a 400 V, 50 Hz, three-phase supply takes a line current of 10 A at an angle of 66.86° lagging with respect to its line voltage. Determine (a) per phase circuit constants, (b) power factor, (c) active, reactive, and apparent powers.</p>	5	3	2