

Midterm Evaluation Scheme

Basic Electronics (ECE-1071) Semester: I Date: 24/09/2024 MARKS:30

1. $\frac{I_o(Ge)}{I_o(Si)} = \frac{(e^{V_{Si}/\eta VT})^{-1}}{(e^{V_{Ge}/\eta VT})^{-1}} = \frac{(e^{0.718/2 \times 26 \times 10^{-3}})^{-1}}{(e^{0.1435/1 \times 26 \times 10^{-3}})^{-1}} = 4 \times 10^3$
2. $V_m = \sqrt{2} \times 200 = 282.84$, $V_{dc} = \frac{2V_m}{\pi} = 180.063$, $I_{dc} = \frac{V_{dc}}{R_L} = 0.18 A$
3. Either of the two options mentioned in (a) and (b)
4. Cut-off region
5. $A_{CL} = \left[1 + \frac{R_f}{R_i}\right] = 2$
6. Derivation- All terms like V, C_{ox}, E L, V(x) etc. need to be explained with/without diagram. All steps to be mentioned.2M

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

a) $V_{DS}=0.8V$, $V_{GS}-V_{th}=3.0-1.0=2.0V$

$$I_{D,lin} = \frac{\mu_p \cdot C_{ox}}{2} \cdot \frac{W}{L} \cdot [2 \cdot (V_{GS} - V_T)V_{DS} - V_{DS}^2]$$

$I_D = 384 \mu A$ 1M

b) Since $V_{DS} = 0.8 V < 2.0$... the MOSFET is in the triode region -1M

7. Breakdown Phenomenon: Avalanche & Zener breakdown - 2M

Effect of Temperature - 1 M

8. $V_d = 0.693$ - 3M

9.

$$\gamma = \frac{V_{rms}}{V_{dc}} = \frac{1}{2\sqrt{3}fCR_L}$$

Ripple factor=0.0103

$$V_{dc} = \frac{2f CR_L}{1+2f CR_L} V_m = 19.65 V (1 M)$$

Circuit Diagram (1M)

10. $I_{zmax} = 20\text{mA}$ ----0.5M
 $I_s = 40\text{mA}$ ---0.5 M
 $I_{Lmin} = 20\text{ mA}$ and $I_{Lmax} = 39\text{ mA}$ ---1M
 $R_{Lmin} = 256.41\ \Omega$ and $R_{Lmax} = 500\ \Omega$ ---1M
11. $V_o = A_d V_d + A_c V_{cm}$; $V_d = 5\text{mV}$; $A_d = 1246$; $V_{cm} = 1\text{mV}$; $A_{cm} = 12$;
CMRR=103.8333; CMRR in dB=40.3267dB
12. $V_m = 31.11\text{V}$
 $I_m = 62.22\text{mA}$ ----- 1/2M
 $I_{dc} = 39.61\text{mA}$ ----- 1/2M
 $I_{rms} = 43.99\text{mA}$ ----- 1/2M
PIV > 62.22V ----- 1/2M
13. Circuit diagram ----- 1/2M
Working ----- 1/2M
 I_{dc} ----- 1/2M
 I_{rms} ----- 1/2M
14. Derivation for V_{out} - 1.5 Marks
Output Voltage = 10V – 0.5Mark