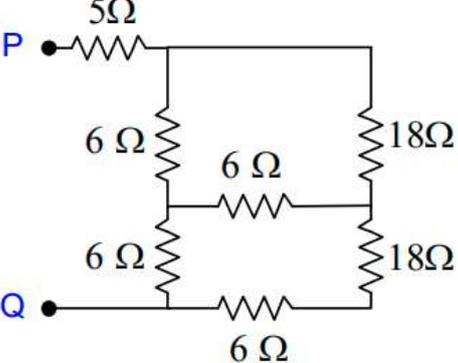
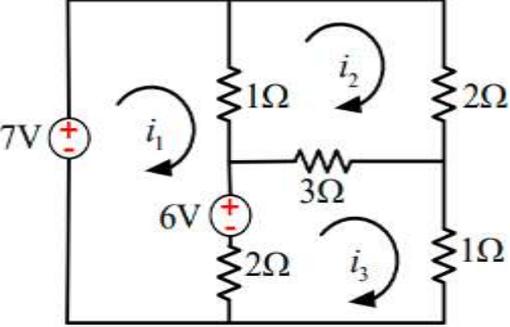
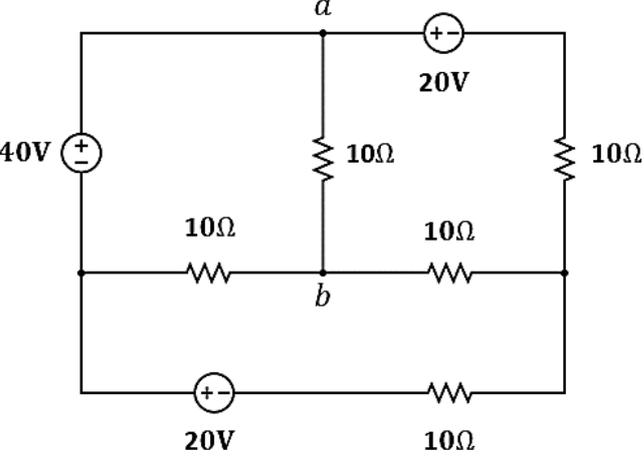
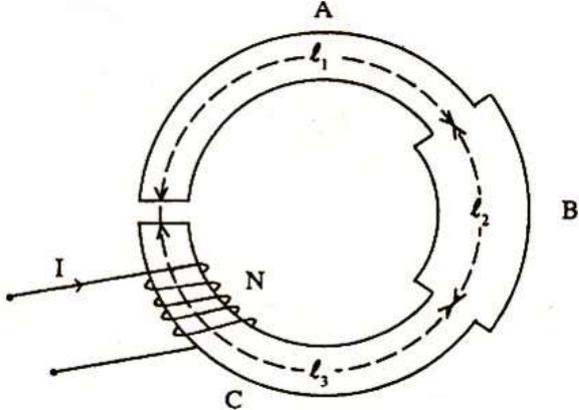
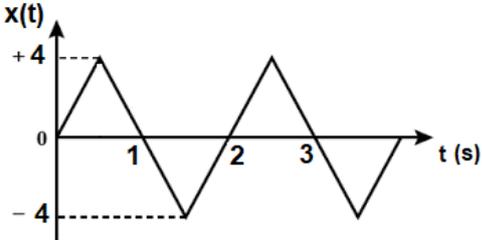
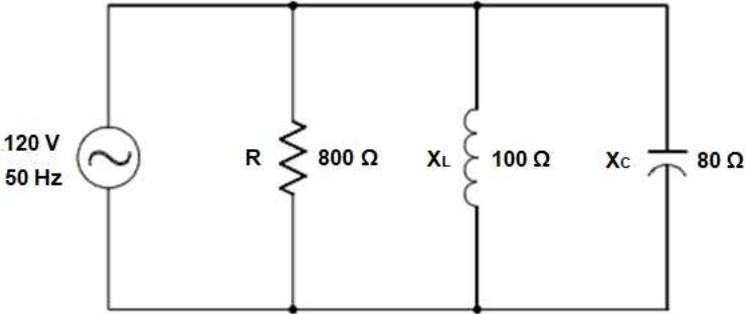
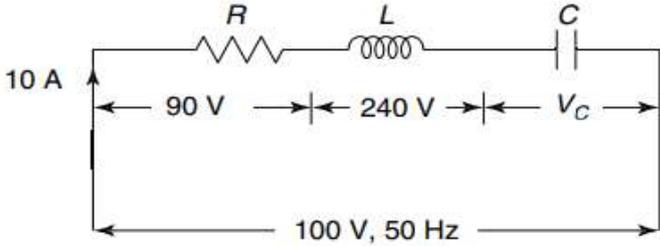


Question Paper – Basic Electrical Technology (ELE 1071) – Makeup Exam – II Sem – 03 July 2023

Q No	Description	Marks	CO	Level
1 A	<p>Determine the input resistance between terminals P & Q of the given network.</p> 	3	1	3
1 B	<p>In the circuit shown, determine the mesh currents i_1, i_2 and i_3.</p> 	3	1	3
1 C	<p>For the given network, determine the current through the resistance 10 Ω connected between points a & b using Thevenin's theorem.</p> 	4	1	3

2 A	<p>A DC supply voltage of 100 V is applied across a relaxed series R-C circuit with C = 5 μF at the time t = 0 s. Find the value of resistance R such that the voltage across the capacitor becomes 50 V in 5 ms after the circuit is switched on. If the series R-C circuit is shorted at 5 ms, what is the capacitor voltage at t = 7 ms?</p>	3	1	3
2 B	<p>The iron ring as shown is made up of three sections A, B and C having a relative permeability of 1000 and has a flux density of 1.8 Tesla in the air gap. For the given dimensions of l₁ = 0.15 m, l₂ = 0.2 m, l₃ = 0.2 m, l_{ag} = 1 cm, A₁ = A₃ = A_{ag} = 2 × 10⁻⁴ m², and A₂ = 3 × 10⁻⁴ m², if the number of turns is 11000, Compute the current through the coil.</p> <p>(Absolute permeability of air = $4\pi \times 10^{-7}$ H/m)</p> 	4	2	3
2 C	<p>There are two inductive coils connected in series in such a way that the net inductance is 2.2 H. When their connections are reversed the total inductance changes to 0.95 H. Find the self-inductances of the two coils. The coefficient of coupling between them is 0.4.</p>	3	2	3
3 A	<p>Determine the RMS value of the following signal.</p> 	3	3	3

3 B	<p>For the given parallel AC circuit, find the total current, power factor and active, reactive & apparent powers.</p> 	3	3	3
3 C	<p>A circuit consists of a pure resistor, a pure inductor, and a capacitor connected in series as shown below. When the circuit is supplied with 100 V, 50 Hz supply, the voltages across inductor and resistor are 240 V and 90 V respectively. If the circuit takes a 10 A leading current, calculate (a) value of inductance, resistance, and capacitance, (b) power factor of the circuit, and (c) voltage across the capacitor.</p> 	4	3	3
4 A	<p>A 1-Φ motor takes 12 A at a power factor of 0.5 lagging from a 240 V, 50 Hz supply. What value must a shunting capacitor have to raise the power factor to 0.9 lagging? Obtain the line current for the new power factor.</p>	4	3	3
4 B	<p>Three similar coils, each of resistance 7 Ω and inductance 0.03 H, are connected in delta to a 400 V, 3-Φ, 50 Hz, RYB system. Assuming V_{RY} as the reference voltage phasor, calculate a) line currents and b) active, reactive, and complex powers.</p>	6	4	3
5 A	<p>The phase of a lightly loaded 3-Φ, 450 V, Δ connected motor draws a current of 13.86 A at a power factor of 0.47 lagging. The two-wattmeter method is used to measure the 3-Φ power supplied to the motor.</p> <p>a) What would each wattmeter read?</p> <p>b) Determine the active and reactive power using wattmeter readings.</p>	4	4	3
5 B	<p>Discuss the function and utility of an electrical substation. List out the major substation components.</p>	3	5	2
5 C	<p>Explain the working principle of a 3-phase induction motor. List their classification.</p>	3	5	2