

Question Paper

Exam Date & Time: 13-Jan-2024 (09:30 AM - 12:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION


FIRST SEMESTER B.TECH. EXAMINATIONS -JANUARY 2024
SUBJECT: ELE 1071 / ELE-1071 - BASIC ELECTRICAL TECHNOLOGY

Marks: 50


Duration: 180 mins.

Answer all the questions.

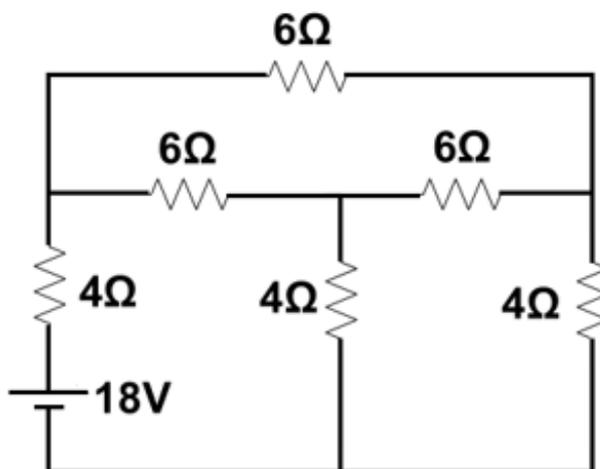
- 1A) Determine the power supplied by the source in the given network. (3)



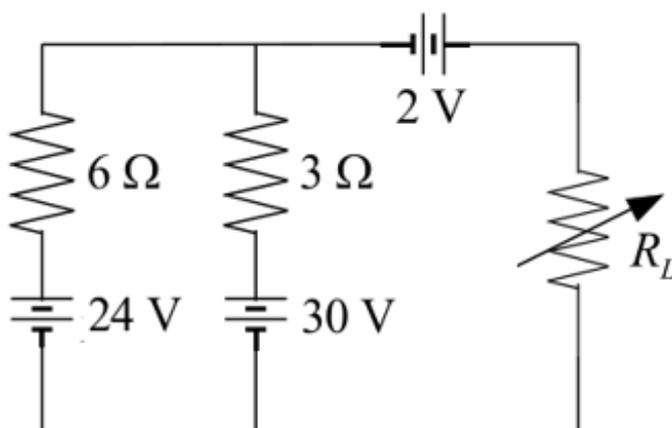
- 1B) Obtain the **maximum power** that could be delivered to the load resistor (R_L), which is variable, in the circuit shown. (3)



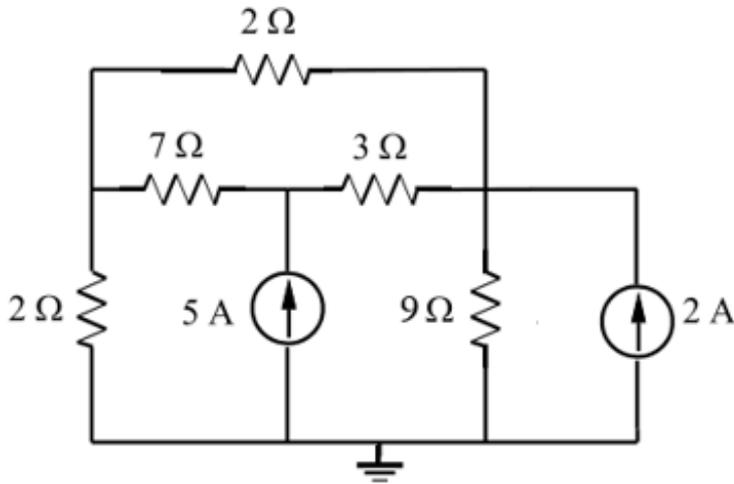
- 1C) Determine the power dissipated in $3\ \Omega$ resistor in the given circuit. (4)



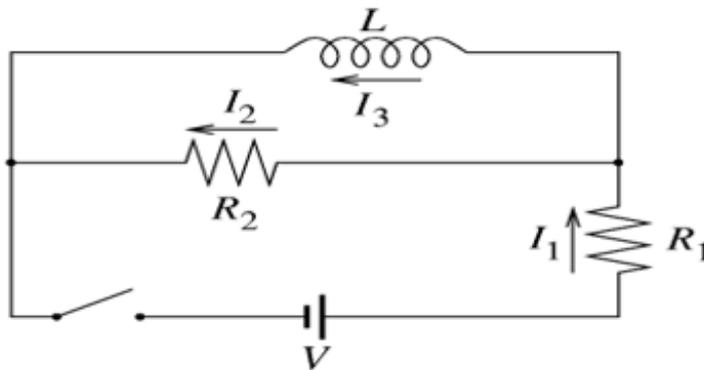
- 2A) The switch in the circuit below has been open for a long time. Determine the currents I_1 , I_2 , and I_3 (3)
 in the resistors and in the **self-inductance (L)**
 i) just after the switch is closed.
 ii) A long time after the switch is closed. The internal resistance of the battery is negligible. Express your answers in terms of V , R_1 , R_2 and L .



- 2B) A ring forming a magnetic circuit is made from two materials; one part is mild steel (relative permeability = **2000**) of mean length **25 cm** and cross-sectional area **4 cm²**, and the remainder is cast iron (relative permeability = **1350**) of mean length **20 cm** and cross-sectional area **7.5 cm²**. Determine the total **MMF** required to cause a flux of **0.30 mWb** in the magnetic circuit. Also find the total reluctance of the circuit. (**Absolute permeability of air = $4\pi \times 10^{-7}$ H/m**) (4)
- 2C) Two coils connected in a series-aiding fashion have a total inductance of **250 mH**. When connected in a series-opposing configuration, the coils have a total inductance of **150 mH**. If the inductance of one coil is three times the other, find the self-inductance of each coil and the mutual inductance. Also, determine the coupling coefficient. (3)
- 3A) Find the **RMS** value of the current signal shown. Also, find the average power consumed if the current signal is fed to a circuit of resistance of **3 Ω**. (3)

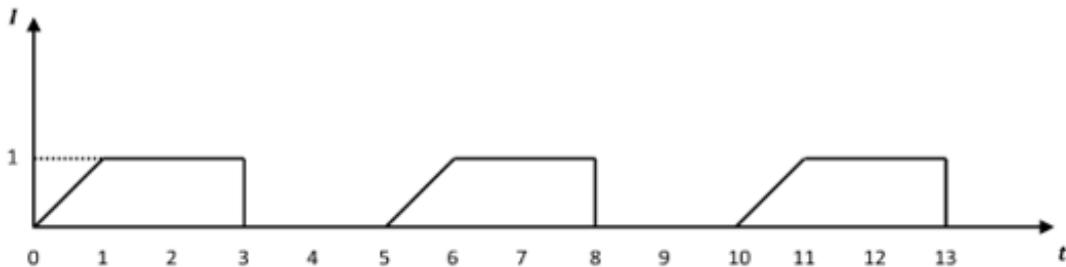


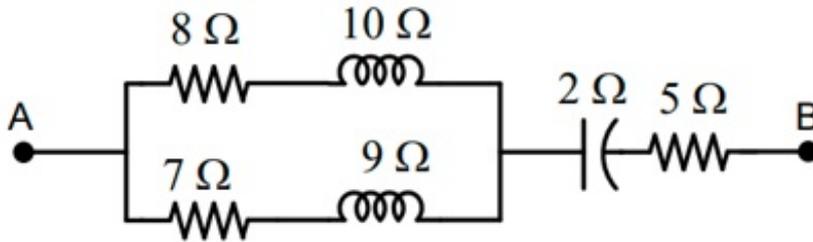- 3B) For the arrangement shown below, determine the impedance between **A & B**, power factor of the circuit and the total power consumed if the applied voltage is **200 ∠ 30°**. (3)



- 3C) In a 1- Φ AC circuit, the two parallel branches **A** and **B** are in series with **C**. The branch impedances are $Z_A = (8 + j 6) \Omega$, $Z_B = (10 - j 8) \Omega$ and $Z_C = (4 + j 2) \Omega$. The voltage across **C** is $(58 + j 0) \text{ V}$. Determine,
 a) Currents I_A , I_B and I_C
 b) Phase angle between currents I_A & I_B and I_A & I_C

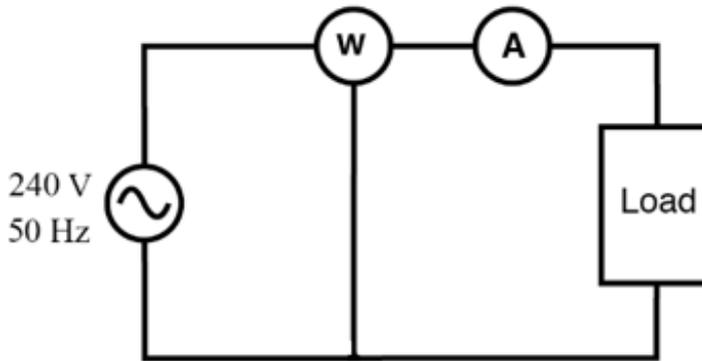- 4A) In the arrangement shown, wattmeter reading (W) = **1.5 kW** and ammeter reading (A) = **9.615 A**. Calculate the value of shunting capacitor required to raise the power factor to **unity**. Obtain the new ammeter reading after power factor correction.



- 4B) Three similar coils, each of resistance **7 Ω** and inductance **0.03 H**, are connected in **delta** to a **400 V, 3- Φ , 50 Hz, RYB** system. Assuming V_{RY} as the reference voltage phasor, calculate a) line currents and b) active, reactive, and complex powers.
- 5A) When connected to a delta-connected load, the two-wattmeter method produces wattmeter readings of **1560 W** and **2100 W**. If the line voltage is **220 V**, calculate,
 i) the per-phase average power
 ii) the per-phase reactive power, and
 iii) the power factor
- 5B) Explain the operation of a transformer. Obtain the expressions for primary and secondary induced EMF in a transformer.
- 5C) Sketch a one-line diagram of a power system network architecture indicating voltage levels at various stages.

-----End-----