



Question Paper



MANIPAL ACADEMY OF HIGHER EDUCATION

B.Tech. First Semester 1st Sessional Examination - November 2022

BASIC ELECTRICAL TECHNOLOGY [ELE 1071]

Marks: 15


Duration: 60 mins.

MCQ

Answer all the questions.

Section Duration: 20 mins

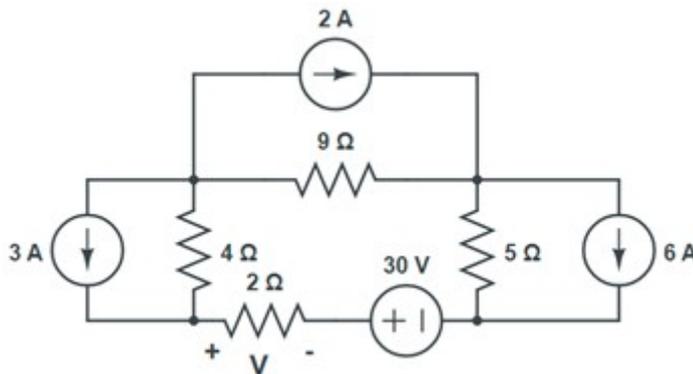
- 1) The value of **voltage V** in the circuit shown is:



(1)

3 V -3 V -6.6 V 6.6 V

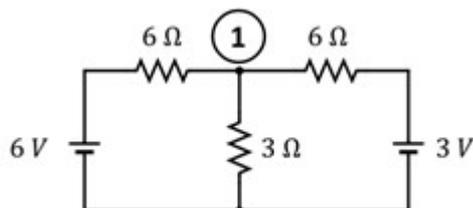- 2) The potential of **Node 1** in the circuit shown is:




(1)

4.5 V 9 V 1.5 V 2.25 V


- 3) For the circuit, with all resistances in **Ohms**, the voltage V_{AF} is:

(1)

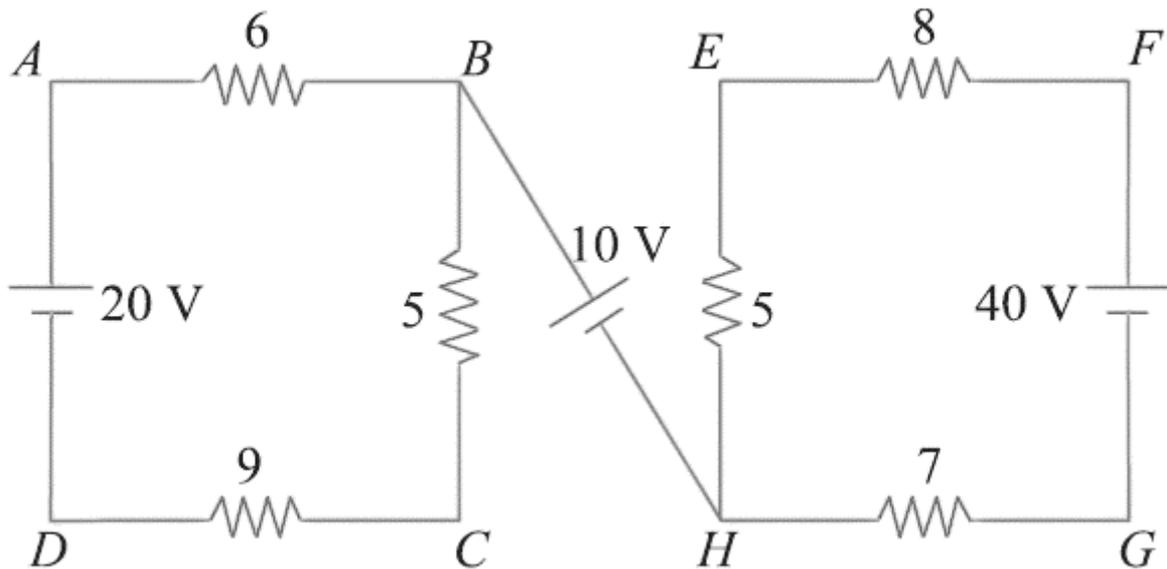

30 V - 10 V 10 V 0 V

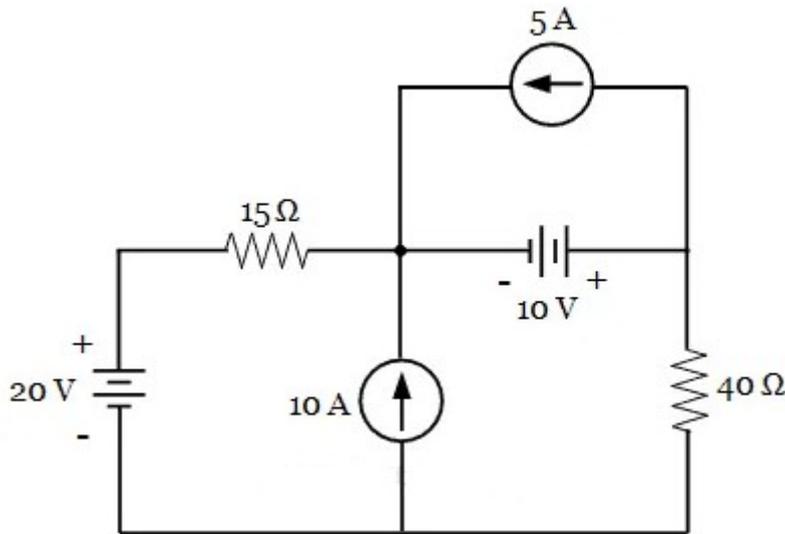- 4) In the circuit shown, based on **superposition** principle, the voltage & current across **15 Ω** resistor due to **5 A** source acting alone are respectively,




(1)

20.45 V & 1.36 A 54.54 V & 3.64 A 0 V and 0 A 75 V & 5 A

- 5) In the circuit shown, the maximum power delivered to the load resistor **R_L** is

(1)

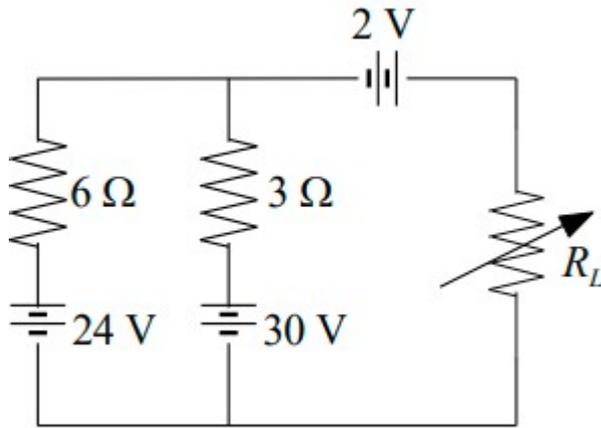


98 W 144.5 W 60.5 W 112.5 W

DESCRIPTIVE


Answer all the questions.

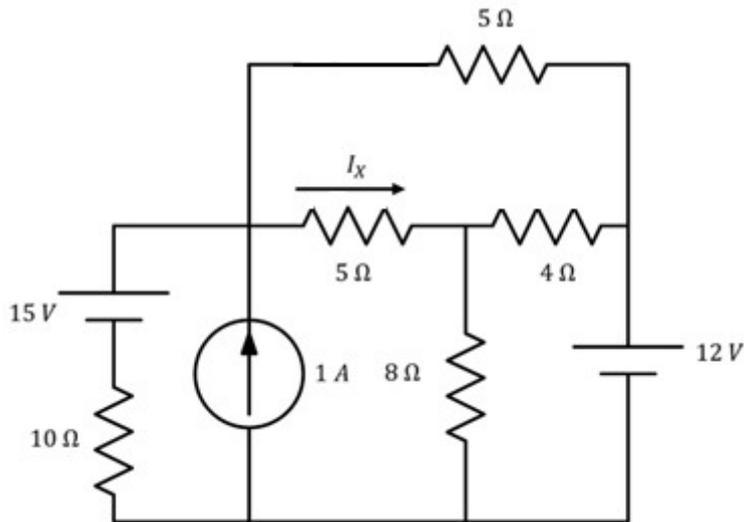- 1) Using **superposition** principle, determine the current I_x as shown.



(4)

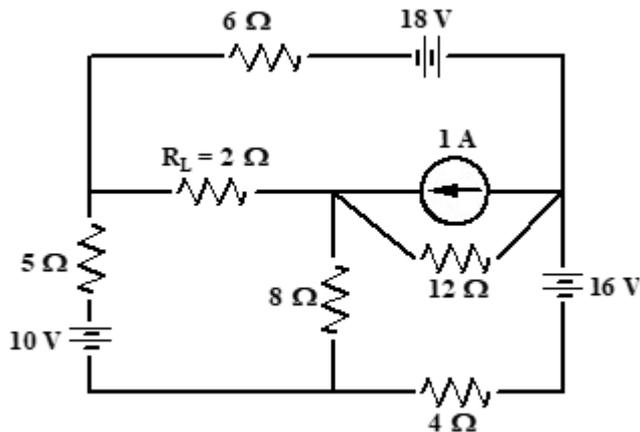- 2) For the circuit shown, find the **Thevenin's** equivalent across the load resistance $R_L = 2\Omega$.



(3)

3)

In the given circuit, the switch was in the closed position for a long time and opened at $t = 0$. Find the current $i(t)$ as shown and the voltage across capacitor, $V_c(t)$ for $t > 0$.

