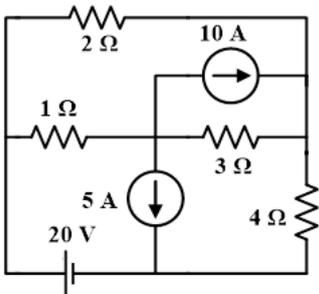


Part A – Objective Questions

Q. No.	Question	Marks
--------	----------	-------

1 The current in the $2\ \Omega$ resistor when only the $20\ \text{V}$ source is acting alone is:


1



- A. 3.75 A
- B. 1.25 A
- C. 3.33 A
- D. 2.5 A**

2 The circuit across terminals **a** and **b** can be represented by a single voltage source (V_{ab}) in series with a resistance (R_{ab}) with the following values:

1

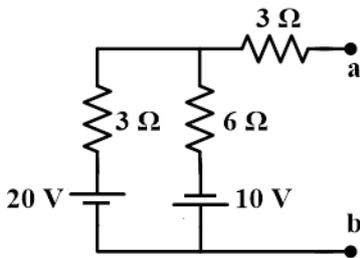

- A. 10 V and $5\ \Omega$**
- B. $-30\ \text{V}$ and $5\ \Omega$
- C. $20\ \text{V}$ and $6\ \Omega$
- D. $-10\ \text{V}$ and $9\ \Omega$

3 A certain $50\ \text{Hz}$ ac circuit draws a current of $(-5 + j10)\ \text{A}$ when the applied voltage is $(50 + j200)\ \text{V}$. The power factor of the circuit is:

1

- A. 0.21 Leading
- B. 0.76 Lagging
- C. Zero
- D. 0.76 Leading**

4 Two separate tests were carried out on a coil. First, when the coil is connected to a $48\ \text{V}$ dc supply, the current flowing through the coil was $4\ \text{A}$. Then, it was connected to $48\ \text{V}$, $50\ \text{Hz}$ ac supply, and the current flowing was $1.6\ \text{A}$. The resistance and the inductance of the coil are, respectively:

1

- A. $30\ \Omega$ and $27.5\ \text{H}$
- B. $12\ \Omega$ and $87.5\ \text{mH}$**
- C. $12\ \Omega$ and $95.5\ \text{mH}$
- D. $27.5\ \Omega$ $38.2\ \text{mH}$

5 A $310\ \mu\text{F}$ capacitor is connected across a $230\ \text{V}$, $50\ \text{Hz}$ ac system. With supply voltage as the reference phasor, the equation of the circuit current is:



1

- A. $31.7 \sin(314t)\ \text{A}$
- B. $22.4 \sin(314t + 90^\circ)\ \text{A}$
- C. $31.7 \sin(314t + 90^\circ)\ \text{A}$**
- D. $31.7 \sin(314t - 90^\circ)\ \text{A}$

Part B – Descriptive Questions

Q. No.	Question	Marks
--------	----------	-------

6	Determine the currents I_1 and I_2 in the given network.	5
---	--	---

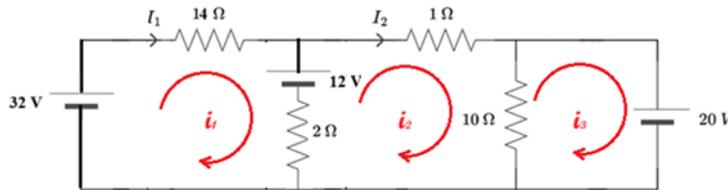
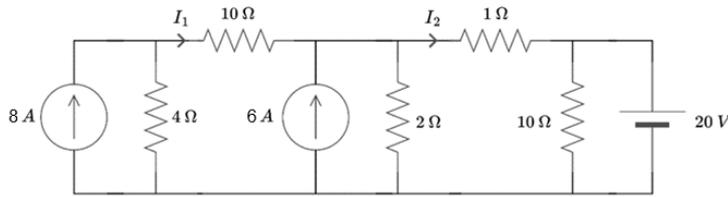


--- 1 M


$$\begin{bmatrix} (14+2) & -2 & 0 \\ -2 & (10+1+2) & -10 \\ 0 & -10 & (10) \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 32-12 \\ 12 \\ -20 \end{bmatrix} \quad \text{--- 3 M}$$

$$I_1 = 1 \text{ A} \quad I_2 = -2 \text{ A} \quad I_3 = -4 \text{ A} \quad \text{--- 1 M}$$

7	Obtain the value of load resistance R_L for maximum power dissipation, and then calculate the maximum power.	5
---	--	---

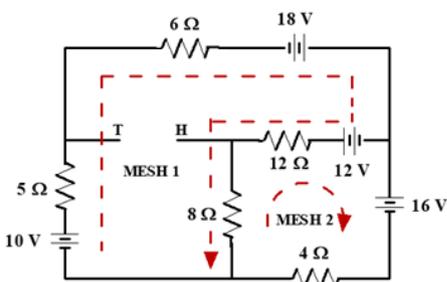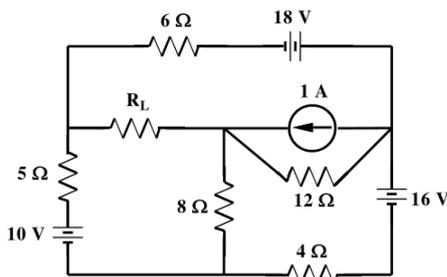

--- 0.5 M

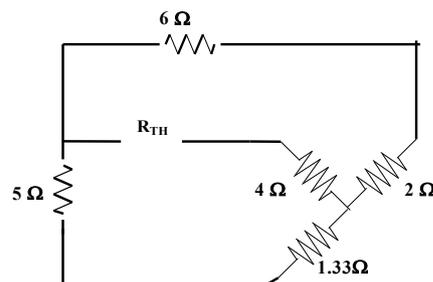

--- 1 M

$$\begin{bmatrix} 31 & -20 \\ -20 & 24 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 40 \\ -28 \end{bmatrix} \quad \text{--- 1.5 M}$$


$$i_1 = 1.1628 \text{ A} \quad \text{and} \quad i_2 = -0.1976 \text{ A} \quad \text{--- 0.5 M}$$

$$V_{Th} = -12(i_2 - i_1) - 12 - 18 + 6i_1 = -6.69 \text{ V} \quad \text{--- 0.5 M}$$

$$R_{Th} = \frac{8 \times 6.33}{8 + 6.33} + 4 = 7.53 \Omega = R_L \quad \text{--- 0.5 M}$$

$$P_{max} = \frac{(6.69)^2}{4 \times 7.53} = 1.486 \text{ W} \quad \text{--- 0.5 M}$$

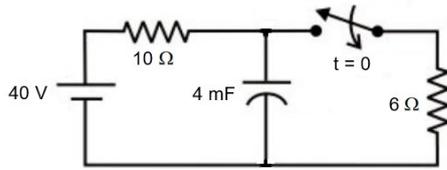- 8 In the given circuit, the switch has been open for a long time and is closed at $t = 0$. Obtain the expression for capacitor voltage for $t > 0$. Determine the time at which the capacitor voltage reaches **25 V**. 4



$$V_c(0^-) = V_c(0) = V_c(0^+) = 40 \text{ V} \quad \text{--- 0.5 M}$$

$$V_c(\text{Final}) = V_{6\Omega} = \left(\frac{40 \times 6}{10 + 6}\right) = 15 \text{ V} \quad \text{--- 0.5 M}$$

$$\tau = [0.004 \times (10 \parallel 6 (= 3.75))] = 15 \text{ ms} \quad \text{--- 1 M}$$

$$v_c(t) = 15 + 25 e^{-66.67 t} \quad \text{--- 1 M}$$

$$t \text{ for } v_c(t) = 25 \text{ V} \Rightarrow 25 = 15 + 25 e^{-66.67 t} \quad \text{--- 0.5 M}$$

$$t = 13.744 \text{ ms for } v_c(t) = 25 \text{ V} \quad \text{--- 0.5 M}$$

- 9 An impedance coil in parallel with a **100 μF** capacitor is connected across a **200 V, 50 Hz**, single-phase ac supply. The coil takes a current of **4 A** and the power loss in the coil is **600 W**. Calculate (i) the resistance of the coil, (ii) the inductance of the coil, (iii) the current drawn by the entire circuit, and (iv) the power factor of the entire circuit. 5

$$Z_{\text{coil}} = \frac{200}{4} = 50 \Omega \quad \text{--- 0.5 M}$$

$$R_{\text{coil}} = \frac{600}{4^2} = 37.5 \Omega \quad \text{--- 0.5 M}$$

$$X_{\text{coil}} = \sqrt{50^2 - 37.5^2} = 33.072 \Omega \quad \text{--- 0.5 M}$$

$$L = \frac{33.072}{2\pi \times 50} = 105.27 \text{ mH} \quad \text{--- 0.5 M}$$

$$\bar{Z}_{\text{coil}} = (37.5 + j 33.072) \Omega = 50 \angle 41.41^\circ \Omega \quad \text{--- 0.5 M}$$


$$\bar{Z}_c = -j \left(\frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}\right) \Omega = 31.831 \angle -90^\circ \Omega \quad \text{--- 0.5 M}$$

$$\bar{Z}_{\text{Total}} = \frac{50 \angle 41.41^\circ \times 31.831 \angle -90^\circ}{50 \angle 41.41^\circ + 31.831 \angle -90^\circ} = (26.99 - j 32.724) \Omega = 42.418 \angle -50.485^\circ \Omega \quad \text{--- 1 M}$$

$$\bar{I} = \frac{200 \angle 0^\circ}{42.418 \angle -50.485^\circ} = 4.715 \angle 50.485^\circ \text{ A} \quad \text{--- 0.5 M}$$

$$\text{PF}_{\text{circuit}} = \cos 50.485^\circ = 0.636 \text{ leading} \quad \text{--- 0.5 M}$$

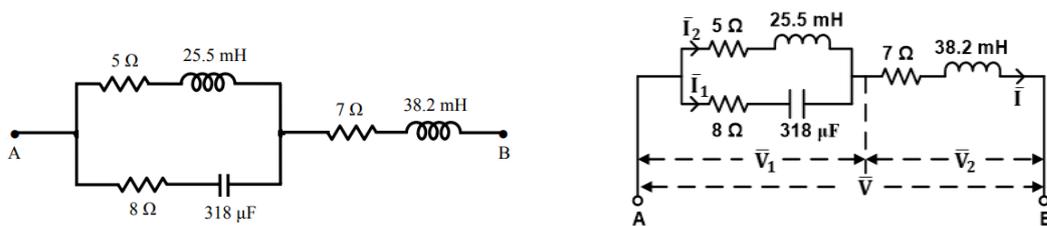- 10 Determine the input voltage at **50 Hz** to be applied to the circuit across terminals **A** and **B**, such that the current in the capacitor is **8 A**. 6



$$\bar{Z}_1 = 8 - j \left(\frac{1}{2\pi \times 50 \times 318 \times 10^{-3}}\right) = (8 - j 10) \Omega = 12.806 \angle -51.34^\circ \Omega \quad \text{--- 0.5 M}$$

$$\bar{Z}_2 = 5 + j (2\pi \times 50 \times 0.0255) = (5 + j 8) \Omega = 9.434 \angle 58^\circ \Omega \quad \text{--- 0.5 M}$$

$$\bar{Z} = 7 + j (2\pi \times 50 \times 0.03852) = (7 + j 12) \Omega = 13.892 \angle 59.744^\circ \Omega \quad \text{--- 0.5 M}$$

$$\bar{V}_1 = 8 \angle 0^\circ \times 12.806 \angle -51.34^\circ = 102.448 \angle -51.34^\circ \text{ V} \quad \text{--- 1 M}$$

$$\bar{I}_2 = \frac{102.448 \angle -51.34^\circ}{9.434 \angle 58^\circ} = 10.859 \angle -109.34^\circ \text{ A} \quad \text{--- 1 M}$$

$$\bar{I} = 8 \angle 0^\circ + 10.859 \angle -109.34^\circ = 11.153 \angle -66.74^\circ \text{ A} \quad \text{--- 1 M}$$

$$\bar{V}_2 = 11.153 \angle -66.74^\circ \text{ A} \times 13.892 \angle 59.744^\circ = 154.937 \angle -7^\circ \text{ V} \quad \text{--- 1 M}$$

$$\bar{V} = 102.448 \angle -51.34^\circ + 154.937 \angle -7^\circ = (217.78 - j 98.88) \text{ V} = 239.18 \angle -24.42^\circ \text{ V} \quad \text{--- 0.5 M}$$