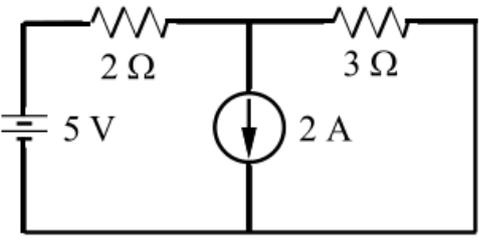
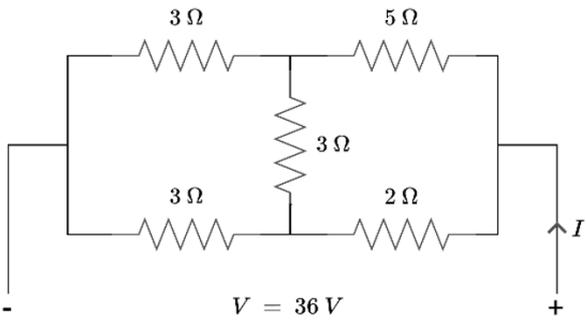
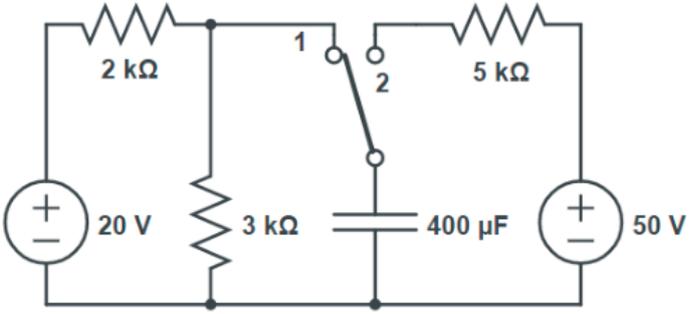


Part A – Objective Questions

Q. No.	Question	Marks	BTL	CO
1	<p>The power dissipated in $2\ \Omega$ resistor in the given circuit is:</p>  <p>a) 0.18 W b) 8 W c) 9.68 W d) 12.5 W</p>	1	3	1
2	<p>The current through $5\ \Omega$ resistor in the given interconnection of resistors is:</p>  <p>a) 12 A b) 8 A c) 3.43 A d) 4 A</p>	1	3	1
3	<p>Initially switch was at position 1 for a long time. It is moved from position 1 to 2 at $t = 0$. The capacitor voltage at $V_c(t = 0)$ and $V_c(t = \infty)$ are respectively,</p>  <p>a) 12 V & 50 V b) 20 V & 50 V c) 0 V & 0 V d) 12 V & 0 V</p>	1	3	1
4	<p>A single-phase AC circuit is represented by the following voltage and current equations: $\bar{V} = 10 \sin(\omega t + 10^\circ)\ \text{V}$ $\bar{I} = 3 \cos(\omega t - 20^\circ)\ \text{A}$ The average power consumed by the circuit is:</p> <p>a) 26 W b) 1.5198 W c) 13 W d) 7.5 W</p>	1	3	2

5	The resulting RMS current in the given circuit is:	1	3	2
a) 3.96 A (Leading)		b) 2.8 A (Leading)		c) 2.8 A (Lagging)
				d) 3.96 A (Lagging)

Part B – Descriptive Questions

Q. No.	Question	Marks	BTL	CO
6	Using superposition principle, determine the current I_x as shown.	5	3	1

$R_{eq} = ((6 + 4) \parallel 8) + 5 + 10 = 19.444 \Omega$

$I = \frac{15}{19.444} = 0.77145 \text{ A}$

$I_x|_{15V} = \frac{0.77145 \times 8}{8 + 10} = 0.3429 \text{ A (A to B)} \quad \text{--- 1 M}$

$I_2 = \frac{1 \times 10}{10 + 9.444} = 0.51428 \text{ A}$

Or $I_x|_{1A} = \frac{(I_2)(8)}{8 + 10} = 0.2286 \text{ A (A to B)} \quad \text{--- 1 M}$

$i_2 = 2 \quad \text{(i)}$


$-23i_1 + 5i_2 + 8i_3 = 0 \quad \text{(ii)}$

$8i_1 + 4i_2 - 18i_3 = 0 \quad \text{(iii)} \quad \text{--- 1.5 M}$


$i_3 = 0.7542 \text{ A}$


$I_x|_{2A} = i_3 - i_2 = -1.2457 \text{ A (A to B)} \quad \text{--- 1 M}$

$I_x = I_x|_{15V} + I_x|_{1A} + I_x|_{2A} = -0.6742 \text{ A} \quad \text{--- 0.5 M}$

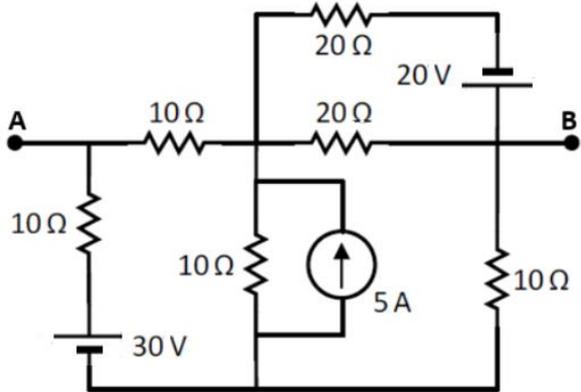
7	<p>Obtain Thevenin's equivalent across the open terminals A & B of the circuit shown. Also determine the maximum possible power available across a load resistance if connected between terminals A & B.</p> 	4	3	1	
---	---	---	---	---	--

One Y - Δ or Δ - Y conversion ----- 0.5 M
 $R_{TH} = 10 \Omega$ ----- 1 M
 $\begin{bmatrix} 30 & -10 \\ -10 & 30 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} -20 \\ 60 \end{bmatrix}$ ----- 1 M
 $i_1 = 0 \text{ A}$ and $i_2 = 2 \text{ A}$ ----- 0.5 M
 $V_{TH} = V_{AB} = (2 \times 10) - 10 = 10 \text{ V}$ ----- 0.5 M
 $P_{Max} = \frac{10^2}{4 \times 10} = 2.5 \text{ W}$ ----- 0.5 M

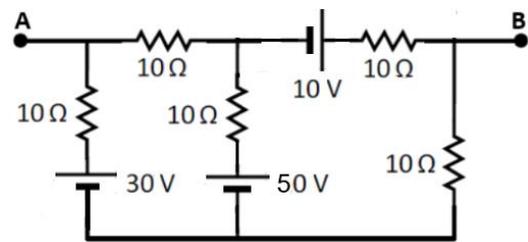

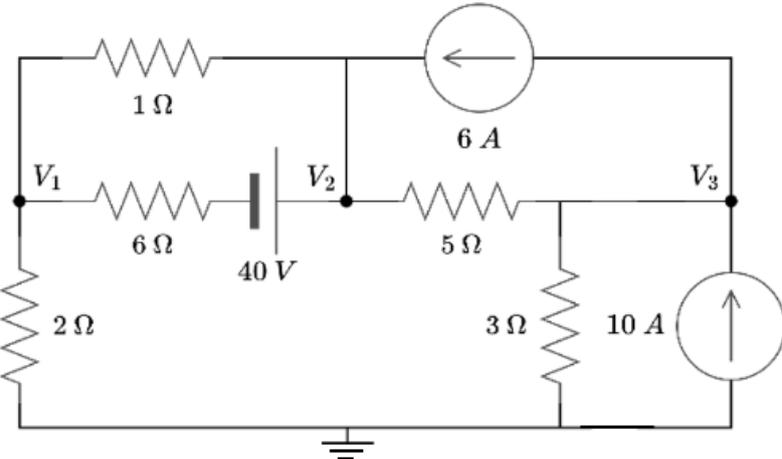
8	<p>Determine the node voltages V_1, V_2, V_3 and power supplied by 6 A source in the given circuit.</p> 	4	4	1	
---	---	---	---	---	--

Source transformation ----- 0.5 M
 $V_1 \left(\frac{1}{6} + \frac{1}{2} + \frac{1}{1} \right) - V_2 \left(\frac{1}{6} + \frac{1}{1} \right) = -\frac{40}{6}$ ----- 1 M
 $-V_1 \left(\frac{1}{6} + \frac{1}{1} \right) + V_2 \left(\frac{1}{6} + \frac{1}{1} + \frac{1}{5} \right) - V_3 \left(\frac{1}{5} \right) = \frac{40}{6} + 6$ ----- 1 M
 $-V_2 \left(\frac{1}{5} \right) + V_3 \left(\frac{1}{5} + \frac{1}{3} \right) = 10 - 6$ ----- 1 M
 $V_1 = 10 \text{ V}, V_2 = 20 \text{ V}, V_3 = 15 \text{ V}$ ----- 0.5 M
 $P_{6A} = (V_2 - V_3) \times 6 = 30 \text{ W}$

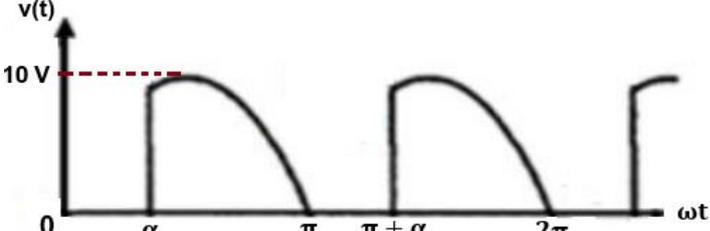9	<p>The output voltage waveform of a single-phase full wave controlled rectifier with sinusoidal input is as shown. Determine the RMS and Average values waveform considering $\alpha = \pi / 3$ radians.</p> 	4	3	2	
---	--	---	---	---	--

$$V_{AVG} = \frac{1}{\pi} \int_{\pi/3}^{\pi} 10 \sin(\omega t) d(\omega t) = 4.755 \text{ V} \quad \text{--- 1.5 M}$$

$$V_{RMS} = \sqrt{\frac{1}{\pi} \int_{\pi/3}^{\pi} (10 \sin(\omega t))^2 d(\omega t)} = 6.342 \text{ V} \quad \text{--- 2.5 M}$$

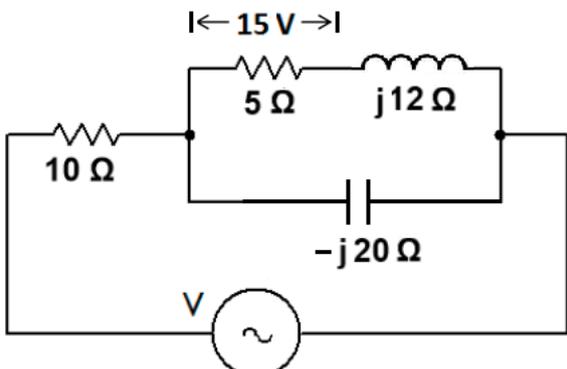10	<p>Obtain the supply voltage (V), total current, and power factor for the given single-phase AC circuit.</p> 	4	3	2	
----	--	---	---	---	--

$$\bar{I}_1 = \frac{15}{5} = 3 \angle 0^\circ \text{ A} \quad \text{--- 0.5 M}$$

$$\bar{V}_{BC} = 3 \angle 0^\circ \times (5 + j12) = 3 \angle 0^\circ \times 13 \angle 67.38^\circ = 39 \angle 67.38^\circ \text{ V} \quad \text{--- 0.5 M}$$

$$\bar{I}_2 = \frac{39 \angle 67.38^\circ}{20 \angle -90^\circ} = 1.95 \angle 157.38^\circ \text{ A} \quad \text{--- 0.5 M}$$


$$\bar{I} = \bar{I}_1 + \bar{I}_2 = 1.415 \angle 32^\circ \text{ A} \quad \text{--- 1 M}$$

$$\bar{V}_{AB} = 1.415 \angle 32^\circ \times 10 \angle 0^\circ = 14.15 \angle 32^\circ \text{ V} \quad \text{--- 0.5 M}$$

$$\bar{V} = 14.15 \angle 32^\circ + 39 \angle 67.38^\circ = 51.197 \angle 58.171^\circ \text{ V} \quad \text{--- 0.5 M}$$

$$\text{PF} = \cos(58.171 - 32)^\circ = 0.8975 \text{ Lagging} \quad \text{--- 0.5 M}$$

11	<p>Two impedances Z_1 and Z_2 are connected in series across 230 V, 50 Hz, single phase AC supply as shown. If the voltage V_1 across Z_1 is $120 \angle 30^\circ$, determine</p> <ol style="list-style-type: none"> The value of impedance Z_2 Net resistance, and inductance & capacitance of the circuit. Power factor of the circuit. Reactive power drawn by the circuit. 	4	4	2	
----	---	----------	----------	----------	--

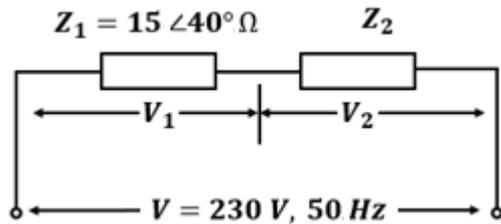

$$\bar{Z}_1 = 15 \angle 40^\circ \Omega = (11.491 + j 9.642) \Omega$$

$$\bar{I} = \frac{120 \angle 30^\circ}{15 \angle 40^\circ} = 8 \angle -10^\circ \text{ A} \quad \text{--- 0.5 M}$$

$$\bar{Z} = \frac{230 \angle 0^\circ}{8 \angle -10^\circ} = 28.75 \angle 10^\circ \Omega = (28.313 + j 50) \Omega \quad \text{--- 0.5 M}$$

$$\bar{Z}_2 = 28.75 \angle 10^\circ - 15 \angle 40^\circ = (16.822 - j 4.649) \Omega = 17.453 \angle -15.449^\circ \Omega \quad \text{--- 1 M}$$

$$\text{Net resistance} = \text{Re}(\bar{Z}) = 28.313 \Omega$$

$$\text{Inductive Reactance } (X_L) = \text{Im}(\bar{Z}_1) = 9.642 \Omega \text{ and Inductance } (L) = 30.69 \text{ mH} \quad \text{--- 0.5 M}$$

$$\text{Capacitive Reactance } (X_C) = \text{Im}(\bar{Z}_2) = 4.649 \Omega \text{ and Capacitance } (C) = 684.684 \mu\text{F} \quad \text{--- 0.5 M}$$

$$\text{PF} = \cos 10^\circ = 0.985 \text{ Lagging} \quad \text{--- 0.5 M}$$

$$Q = 230 \times 8 \times \sin 10^\circ = 319.513 \text{ VAR (Lagging)} \quad \text{--- 0.5 M}$$