
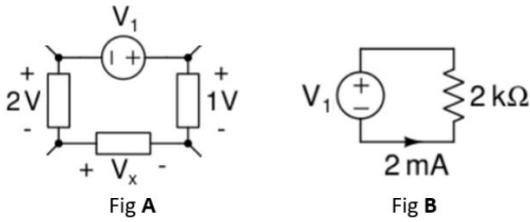


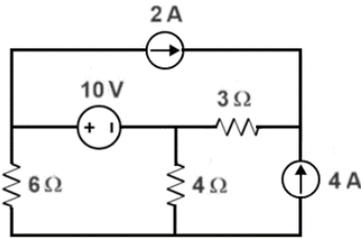
- 1 The voltage source V_1 is such that when it is connected to a $2\text{ k}\Omega$ resistor, a current of 2 mA flows as shown in the Fig. B. In the Fig. A, the voltage V_x is:



- a) 5 V b) -5 V c) -3 V **d) 3 V**
- 2 The current through $6\ \Omega$ resistor in the given circuit is:



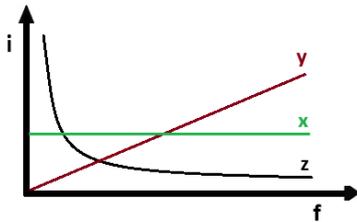
- a) 2 A (bottom to top) **b) 2.6 A (top to bottom)** c) 2.6 A (bottom to top) d) 4 A (top to bottom)
- 3 Three identical voltage sources are connected (separately) to a single circuit element: a resistor, a capacitor, and an inductor. The current amplitude is then measured as a function of frequency. Which one of the following curves corresponds to an **inductive** circuit?



- a) x
b) y
c) z
d) Can't be ascertained with given information
- 4 In an AC circuit, the supply voltage and resulting current are expressed by:
 $\bar{V} = 100 \sin(100\pi t + 24^\circ)\text{ V}$
 $\bar{I} = 5 \cos(100\pi t + 5^\circ)\text{ A}$
 The impedance of the load as well as its nature is
- a) $18.9 - j 6.5\ \Omega \rightarrow$ Leading load
 b) $18.9 + j 6.5\ \Omega \rightarrow$ Lagging load
 c) $6.5 + j 18.9\ \Omega \rightarrow$ Lagging load
d) $6.5 - j 18.9\ \Omega \rightarrow$ Leading load
- 5 A sinusoidal AC voltage of $110 \angle 0^\circ\text{ V}$ is applied across a series **RLC** circuit with $R = 100\ \Omega$, $X_L = 10\ \Omega$ and $X_C = 40\ \Omega$. The **reactive** power of the circuit is:

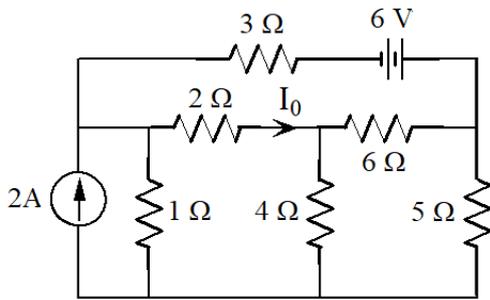- a) 33.3 VAR (Leading)** b) 111 VAR (Leading) c) 33.3 VAR (Lagging) d) 116 VAR (Lagging)

6 Using **superposition** principle, determine the current I_0 as shown.



With 6 V source alone

$$\begin{bmatrix} 7 & -4 & -2 \\ -4 & 15 & -6 \\ -2 & -6 & 11 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 6 \end{bmatrix} \quad \text{--- 1.5 M}$$

$$i_1 = 0.5674 \text{ A}, \quad i_2 = 0.5254 \text{ A}, \quad i_3 = 0.9352 \text{ A}$$

$$I_{0:6V} = (i_1 - i_3) = -0.3678 \text{ A} \quad \text{--- 0.5 M}$$

With 2 A source alone

$$\begin{bmatrix} 7 & -4 & -2 \\ -4 & 15 & -6 \\ -2 & -6 & 11 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix} \quad \text{--- 1.5 M}$$


$$i_1 = 0.45184 \text{ A}, \quad i_2 = 0.19615 \text{ A}, \quad i_3 = 0.18914 \text{ A}$$

$$I_{0:2A} = (i_1 - i_3) = 0.2627 \text{ A} \quad \text{--- 0.5 M}$$

$$I_0 = I_{0:6V} + I_{0:2A} = -0.1051 \text{ A} \quad \text{--- 1 M}$$

7 For the network shown, determine

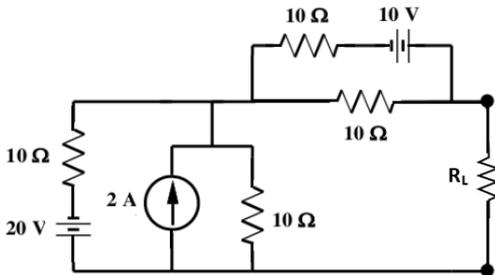- The value of R_L that absorbs maximum power from the circuit.
- The corresponding power under the above condition.




$$V_{Th} = -(2 \times 10) + 20 + (10 \times 0.5) = 5 \text{ V} \quad \text{--- 2 M}$$

$$\text{For } P_{max}: R_L = R_{Th} = (10 \parallel 10) + (10 \parallel 10) = 10 \Omega \quad \text{--- 1.5 M}$$

$$P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = 0.625 \text{ W} \quad \text{--- 0.5 M}$$

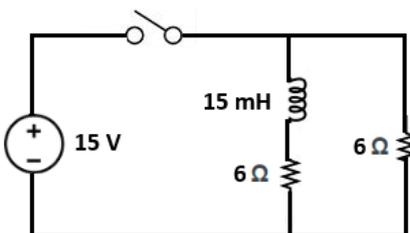8 In the circuit shown, the switch was initially open for a long. It is closed at $t = 0$. Obtain inductor current at $t > 0$. Also determine the value of inductor current after 2 time constant.



$$i_L(\text{initial}) = 0 \text{ A (switch open)} \quad \text{--- 0.5 M}$$


$$i_L(\text{steady}) = 2.5 \text{ A (switch closed)} \quad \text{--- 0.5 M}$$

$$\tau = 0.015/6 = 2.5 \text{ ms} \quad \text{--- 1 M}$$

$$i_L(t) = 2.5(1 - e^{-400t}) \text{ A} \quad \text{--- 1 M}$$

$$i_L(5 \text{ ms}) = 2.162 \text{ A} \quad \text{--- 1 M}$$

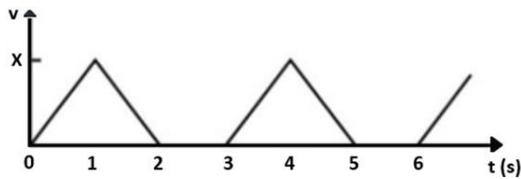- 9 Obtain the **Average** and **RMS** values of the voltage waveform below if the amplitude (**X**) is **10 V**.




$$\text{Equation: } \left\{ \begin{array}{ll} v = 10t & 0 < t < 1 \\ v = 20 - 10t & 1 < t < 2 \\ v = 0 & 2 < t < 3 \end{array} \right\} \quad \text{--- 1 M}$$

$$V_{AVG} = \frac{1}{3} \left[\int_0^1 (10t) dt + \int_1^2 (20 - 10t) dt + \int_2^3 (0) dt \right] = 3.333 \text{ V} \quad \text{--- 1.5 M}$$

$$V_{RMS} = \sqrt{\frac{1}{3} \left[\int_0^1 (10t)^2 dt + \int_1^2 (20 - 10t)^2 dt + \int_2^3 (0)^2 dt \right]} = 4.714 \text{ V} \quad \text{--- 1.5 M}$$

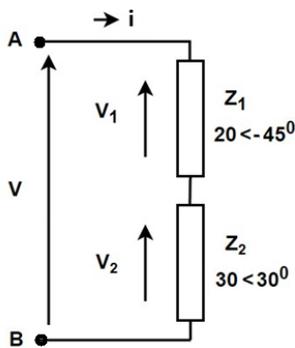- 10 Two impedances of $20 \angle -45^\circ \Omega$ and $30 \angle 30^\circ \Omega$ are connected in series across a certain supply and the resulting current (**i**) is found to be **10 A**. If the supply voltage remains unchanged, obtain the supply current when the impedances are connected in parallel.



$$\text{Let } \bar{I} = 10 \angle 0^\circ \text{ A} \quad \text{--- 0.5 M}$$

$$\bar{Z}_T = (\bar{Z}_1 + \bar{Z}_2) = 40.132 \angle 1.225^\circ \Omega \quad \text{--- 1 M}$$

$$\bar{V} = \bar{I} \times \bar{Z}_T = 401.32 \angle 1.225^\circ \text{ V} \quad \text{--- 0.5 M}$$

$$\bar{Z}_{T-\text{New}} = \frac{\bar{Z}_1 \bar{Z}_2}{\bar{Z}_1 + \bar{Z}_2} = 14.951 \angle -16.225^\circ \Omega \quad \text{--- 1.5 M}$$

$$\bar{I}_{\text{New}} = \frac{\bar{V}}{\bar{Z}_{T-\text{New}}} = 26.842 \angle 17.45^\circ \text{ A} \quad \text{--- 0.5 M}$$

- 11 A **240 V, 50 Hz** source supplies a parallel combination of a **5 KW** heater and a **25 KVA** induction motor whose power factor is **0.82** lagging. Determine:
- the system apparent power
 - the system reactive power, and
 - the value of the capacitor required to adjust the system power factor to **0.95** lagging.

$$P_1 = 5 \text{ KW}$$

$$P_2 = S_2 \cos \phi_2 = 25 \times 0.82 = 20.5 \text{ KW}$$

$$P_T = 25.5 \text{ KW} \quad \text{--- 0.5 M}$$

$$Q_1 = 0 \text{ KVAR}$$

$$Q_2 = 25 \times \sin(\cos^{-1} 0.82) = 14.31 \text{ KVAR}$$

$$Q_T = 14.31 \text{ KVAR (Lagging)} \quad \text{--- 0.5 M}$$

$$S_T = \sqrt{25.5^2 + 14.31^2} = 29.241 \text{ KVA} \quad \text{--- 1 M}$$

$$\cos \phi_{\text{New}} = 0.95 \text{ Lagging} \quad \text{or } \phi_{\text{New}} = 18.195^\circ$$

$$Q_{\text{New}} = 25.5 \times \tan 18.195^\circ = 8.3815 \text{ KVAR (Lagging)} \quad \text{--- 0.5 M}$$

$$Q_C = Q_T - Q_{\text{New}} = 5.9285 \text{ KVAR (Leading)} \quad \text{--- 0.5 M}$$

$$X_C = \frac{240^2}{Q_C} = 9.716 \Omega \quad \text{--- 0.5 M}$$

$$C = \frac{1}{2\pi f X_C} = 327.614 \mu\text{F} \quad \text{--- 0.5 M}$$